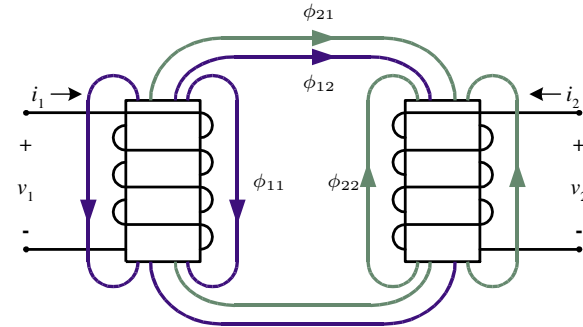


Magnetically Coupled Circuits Overview


- Mutual Inductance
- Energy in Coupled Coils
- Linear Transformers
- Ideal Transformers

Introduction to Magnetically Coupled Circuits



- Magnetically coupled coils are conceptually similar to two inductors that have a shared (coupled) magnetic field
- Not all of the magnetic field is shared
- Magnetic coupling is widely used in power systems

Magnetically Coupled Coil

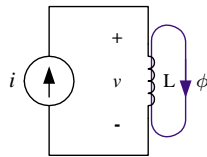


Faraday's Law:

where

$$\begin{aligned}
 v &= N \frac{d\phi}{dt} \\
 \phi &= N \mathcal{P} i \\
 v &= N \frac{d\phi}{di} \frac{di}{dt} \\
 &= N^2 \mathcal{P} \frac{di}{dt} \\
 &= L \frac{di}{dt}
 \end{aligned}
 \quad
 \begin{aligned}
 v &= \text{voltage in volts (V)} \\
 N &= \text{number of turns} \\
 \phi &= \text{magnetic flux in webers (Wb)} \\
 t &= \text{time in seconds (s)} \\
 \mathcal{P} &= \text{permeance of the flux space} \\
 i &= \text{current in amperes (A)} \\
 L &= \text{inductance in henrys (H)}
 \end{aligned}$$


Magnetically Coupled Coil

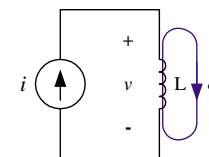

$$v = N \frac{d\phi}{dt} = (N^2 \mathcal{P}) \frac{di}{dt} = L \frac{di}{dt}$$

- The flux (& current) have to change to induce a voltage
- The relationship between the flux and the current is constant
- Consistent with what we already know about inductors
- L is proportional to N^2


Mutual Inductance

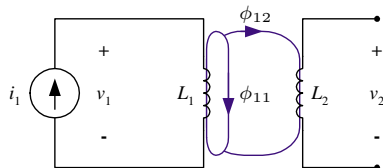

$$\phi_1 = \phi_{11} + \phi_{12}$$


- We can decompose the magnetic flux induced in one coil into two components
- ϕ_1 is the total flux produced in coil 1
- ϕ_{11} is the portion of this flux that links only coil 1
- ϕ_{12} links both coil 1 and coil 2
- The coils are not connected electrically

Mutual Inductance Continued

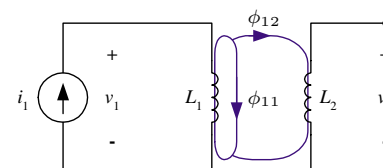

$$\begin{aligned} v_1 &= N_1 \frac{d\phi_1}{dt} &= N_1 \frac{d\phi_1}{di_1} \frac{di_1}{dt} &= L_1 \frac{di_1}{dt} \\ v_2 &= \pm N_2 \frac{d\phi_{12}}{dt} &= \pm N_2 \frac{d(N_1 \mathcal{P}_{12} i_1)}{dt} &= \pm (N_2 N_1 \mathcal{P}_{12}) \frac{di_1}{dt} \\ &= \pm M_{21} \frac{di_1}{dt} \end{aligned}$$


Mutual Inductance Continued 2

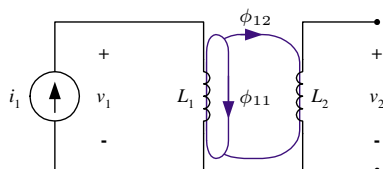

$$v_1 = L_1 \frac{di_1}{dt} \quad v_2 = \pm M_{21} \frac{di_1}{dt} \quad M_{21} = N_2 N_1 \mathcal{P}_{12}$$

- M_{21} : the mutual inductance of coil 2 with respect to coil 1
- Note that v_2 is the open circuit voltage
- What if a current was applied to coil 2 as well?
- Superposition applies


Mutual Inductance: Two Sources

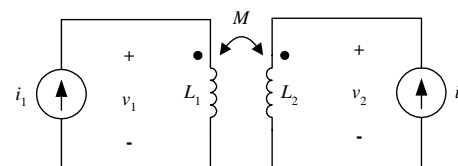

$$\begin{aligned} v_1 &= L_1 \frac{di_1}{dt} \pm M_{12} \frac{di_2}{dt} \\ v_2 &= \pm M_{21} \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{aligned}$$


- We will assume $M_{21} = M_{12} = M$
- If assumption holds, the coils are called a *linear transformer*
- M is called the mutual inductance
- Measured in henrys (H)
- Polarity of coupling term depends on how the coils are wound

Linear Transformer: The Dot Convention

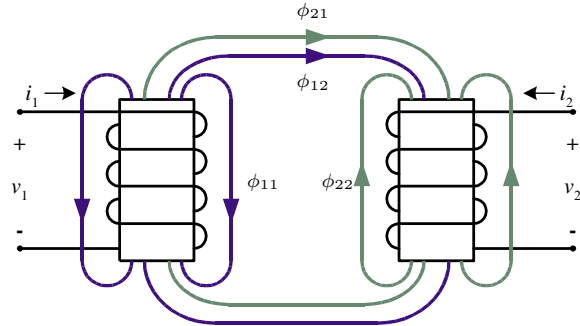


- The dot convention determines the polarity of the coupling
- If a current *enters* a dotted terminal, it induces a *positive* voltage at the dotted terminal of the second coil
- If a current *leaves* a dotted terminal, it induces a *negative* voltage at the dotted terminal of the second coil

Example 1: The Dot Convention

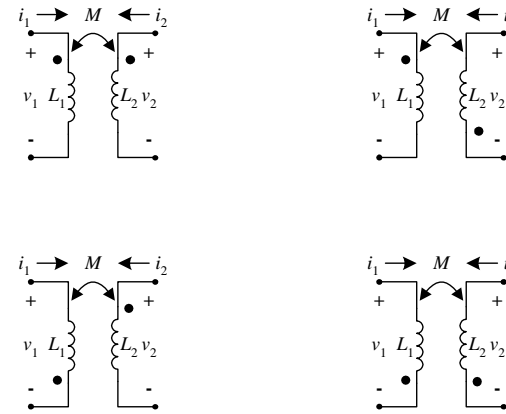

Write the defining equations for each of the circuits shown above.

Example 2: The Dot Convention

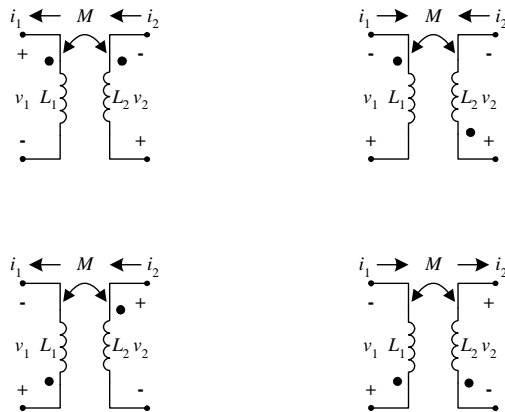

Write the defining equations for each of the circuits shown above.

Mutual Inductance & Self Inductance

$$L_1 = N_1^2 \mathcal{P}_1 \quad \mathcal{P}_1 = \mathcal{P}_{11} + \mathcal{P}_{12}$$

$$L_2 = N_2^2 \mathcal{P}_2 \quad \mathcal{P}_2 = \mathcal{P}_{22} + \mathcal{P}_{21}$$

$$L_1 L_2 = N_1^2 N_2^2 \mathcal{P}_1 \mathcal{P}_2$$

$$L_1 L_2 = N_1^2 N_2^2 (\mathcal{P}_{11} + \mathcal{P}_{12})(\mathcal{P}_{22} + \mathcal{P}_{21})$$

Since $M_{12} = M_{21}$ for a linear system, $\mathcal{P}_{12} = \mathcal{P}_{21}$ and

$$L_1 L_2 = N_1^2 N_2^2 \mathcal{P}_{12}^2 \left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right)$$

$$= M^2 \frac{1}{k^2}$$

$$M = k \sqrt{L_1 L_2}$$

Coefficient of Coupling (k)

$$\frac{1}{k^2} = \left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right)$$

$$M = k\sqrt{L_1 L_2}$$

- k is called the *coefficient of coupling*
- Since $\frac{1}{k^2} \geq 1$, $k \leq 1$
- k is non-negative since $\mathcal{P} > 0$
- If two coils have no common flux, $k = 0$
- If both coils share *all* flux, $k = 1$
- It is physically impossible for $k = 1$, but some magnetic cores have k very close to 1

Linear Transformers: Energy

Suppose no energy is stored in the coils at $t = 0$ and over some period of time t_1 the current in coil 1 increases from 0 to I_1 while the current in coil 2 is zero, $i_2 = 0$. The energy stored in the coils over this period is given by

$$w_1 = \int_0^{t_1} v_1 i_1 d\tau = \int_0^{t_1} \left(L \frac{di_1}{d\tau} \right) i_1 d\tau = L_1 \int_0^{I_1} i_1 di_1 = \frac{1}{2} L_1 I_1^2$$

Now suppose the current in coil 1 is held constant, $i_1 = I_1$, while the current in coil 2 increases from 0 to I_2 .

$$\begin{aligned} v_1 &= L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} &= \pm M \frac{di_2}{dt} \\ v_2 &= \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} &= L_2 \frac{di_2}{dt} \\ p_2 &= v_1 I_1 + v_2 i_2 &= \pm M \frac{di_2}{dt} I_1 + L_2 \frac{di_2}{dt} i_2 \end{aligned}$$

Linear Transformers: Energy Continued


The energy stored in the coils during the second period is given by

$$\begin{aligned} w_2 &= \int_{t_1}^{t_2} p_2 d\tau \\ &= \int_{t_1}^{t_2} \left(\pm M \frac{di_2}{d\tau} I_1 + L_2 i_2 \frac{di_2}{d\tau} \right) d\tau \\ &= \pm M I_1 \int_0^{I_2} di_2 + L_2 \int_0^{I_2} i_2 di_2 \\ &= \pm M I_1 I_2 + \frac{1}{2} L_2 I_2^2 \end{aligned}$$

Then the total energy stored in magnetically coupled coils after the currents have been applied is given by

$$\begin{aligned} w &= w_1 + w_2 \\ &= \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2 \end{aligned}$$


Linear Transformers: Energy Comments

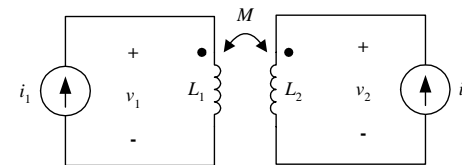

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

- The polarity of the shared term depends on how the coils are wound
- Can the energy stored ever be negative?
- Recall that $M = k\sqrt{L_1 L_2}$
- This limits the expression above to non-negative values only

Time-Domain Analysis

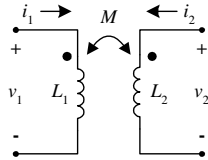

Time Domain

$$\begin{aligned} v_1 &= L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} \\ v_2 &= \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{aligned}$$

What is v_1 if $i_1 = A_1 \cos(\omega t)$ and $i_2 = 0$?

Sinusoidal Steady-State Analysis

What is v_1 if $i_1 = A_1 \cos(\omega t)$ and $i_2 = 0$?


$$\begin{aligned} v_1 &= L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} & v_2 &= \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \\ v_1 &= L_1 \frac{di_1}{dt} & v_2 &= \pm M \frac{di_1}{dt} \\ v_1 &= \omega L_1 A_1 (-\sin(\omega t)) & v_2 &= \pm \omega M A_1 (-\sin(\omega t)) \\ v_1 &= \omega L_1 A_1 \cos(\omega t + 90^\circ) & v_2 &= \pm \omega M A_1 \cos(\omega t + 90^\circ) \end{aligned}$$

What is the relationship in the phasor domain?

$$V_1 = j\omega L_1 I_1 \quad V_2 = \pm j\omega M I_1$$

Superposition applies so if $i_2 = A_2 \cos(\omega t)$,

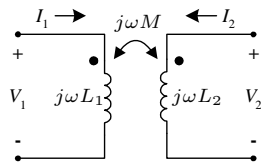Sinusoidal Steady-State Analysis Continued




Frequency Domain (Phasors)

$$\begin{aligned} V_1 &= j\omega L_1 I_1 + j\omega M I_2 \\ V_2 &= j\omega M I_1 + j\omega L_2 I_2 \end{aligned}$$

The dot convention still applies (not shown)

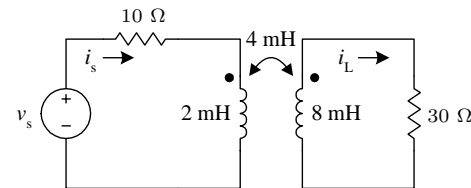
Example 3: Linear Transformers & Phasor Analysis



Find the steady-state expressions for the currents i_s and i_L when $v_s = 70 \cos(5000t)$ V.

Example 3: Workspace

Phasor Analysis: T-Equivalent

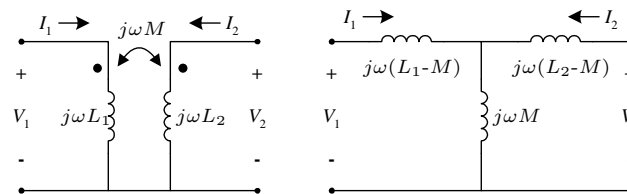


Frequency Domain (Phasors)

$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$


- The T-equivalent is only valid if bottom terminals are connected
- There is also a Π -equivalent (see text)

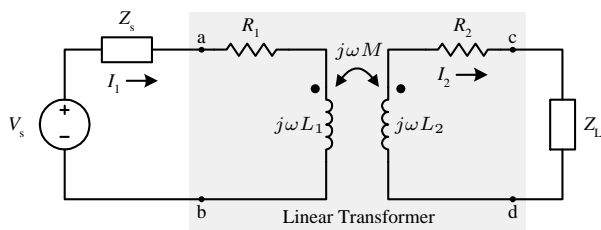Linear Transformer Analysis: Typical Configuration




- Transformers are typically used in only few types of circuits
- The most common configuration connects a source to a load
- Useful to decrease (or increase) the voltage across the load
- Why not just use a voltage divider?
- Should know how to analyze this type of circuit thoroughly

Linear Transformer: Source-Load Analysis

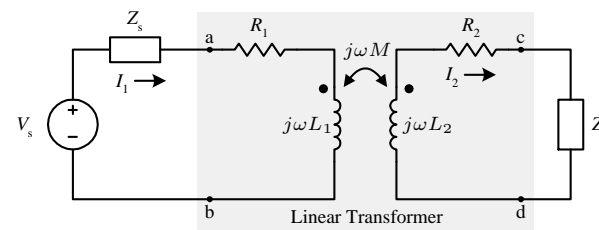

- R_1 = Resistance of primary winding
- R_2 = Resistance of secondary winding
- L_1 = Self-inductance of primary
- L_2 = Self-inductance of secondary
- M = Mutual inductance
- Z_s = Source impedance
- Z_L = Load impedance

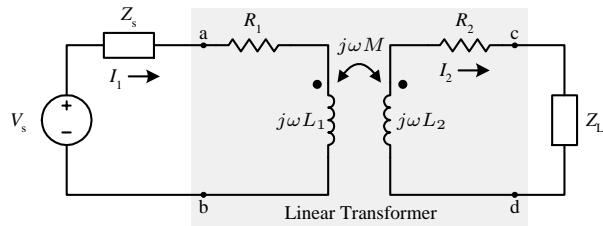Linear Transformer: Source–Load Analysis Continued




$$\begin{aligned} V_s &= (Z_s + R_1 + j\omega L_1)I_1 - j\omega M I_2 \\ 0 &= -j\omega M I_1 + (R_2 + j\omega L_2 + Z_L)I_2 \\ Z_{11} &\triangleq Z_s + R_1 + j\omega L_1 \\ Z_{22} &\triangleq R_2 + j\omega L_2 + Z_L \\ V_s &= Z_{11}I_1 - j\omega M I_2 \\ 0 &= -j\omega M I_1 + Z_{22}I_2 \end{aligned}$$

Linear Transformer: Source–Load Analysis Continued 2


$$\begin{aligned} V_s &= Z_{11}I_1 - j\omega M I_2 \\ 0 &= -j\omega M I_1 + Z_{22}I_2 \\ I_2 &= \frac{j\omega M}{Z_{22}}I_1 \\ V_s &= \left(Z_{11} + \frac{\omega^2 M^2}{Z_{22}} \right) I_1 \\ I_1 &= \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} V_s \\ I_2 &= \frac{j\omega M}{Z_{11}Z_{22} + \omega^2 M^2} V_s \end{aligned}$$

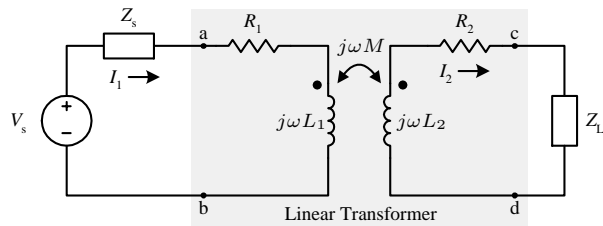Linear Transformer: Source–Load Internal Impedance




$$\begin{aligned} Z_i &\triangleq \frac{V_s}{I_1} = \frac{Z_{11}Z_{22} + \omega^2 M^2}{Z_{22}} \\ &= Z_{11} + \frac{\omega^2 M^2}{Z_{22}} \\ Z_{ab} &= Z_i - Z_s = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{Z_{22}} \end{aligned}$$

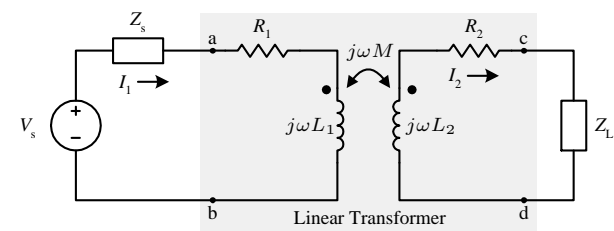Linear Transformer: Source–Load Reflected Impedance



$$\begin{aligned} Z_{ab} &= R_1 + j\omega L_1 + \frac{\omega^2 M^2}{Z_{22}} \\ Z_R &= Z_{ab} - (R_1 + j\omega L_1) \\ &= \frac{\omega^2 M^2}{Z_{22}} = \frac{\omega^2 M^2}{|Z_{22}|^2} Z_{22}^* \end{aligned}$$

Example 4: Linear Transformers

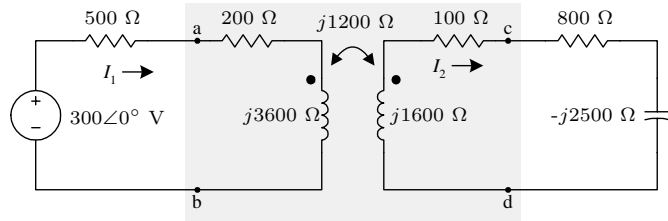


Find the following:

1. Self-impedance of primary & secondary circuits
2. Impedance reflected into the primary winding
3. Impedance seen looking into the primary terminals of the transformer
4. Thévenin equivalent with respect to the terminals c,d

Example 4: Workspace

Example 5: Linear Transformers

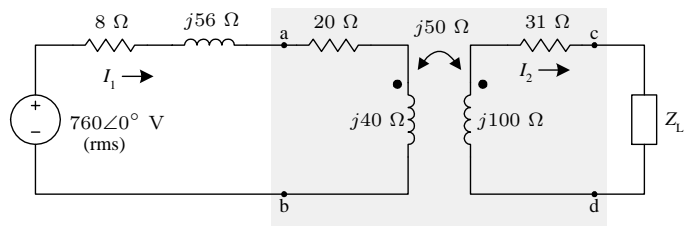


Find the following:

1. Thévenin equivalent with respect to the terminals c,d
2. If Z_L is set equal to Z_{eq}^* , what is I_1 ?
3. What is I_2 ?

Example 5: Workspace (1)


Example 5: Workspace (2)

Introduction to Ideal Transformers

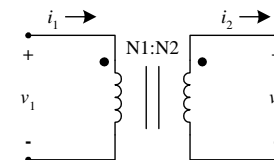


- Ideal/Linear transformers are similar to ideal/real models of operational amplifiers
- Both ideal models make assumptions that simplify analysis
- Ideal approximation: all of the flux links both coils
- Ideal Assumptions
 - Large reactance: $L_1, L_2, M \rightarrow \infty$
 - Perfect coupling: $k \rightarrow 1$
 - Primary and secondary are lossless: $R_1 = R_2 = 0$

Ideal Transformer Analysis

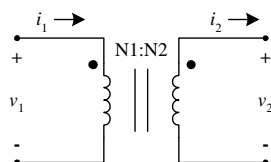

$$\begin{aligned}
 v_1 &= N_1 \frac{d\phi}{dt} & p_1 &= p_2 \\
 v_2 &= N_2 \frac{d\phi}{dt} & v_1 i_1 &= v_2 i_2 \\
 \frac{v_2}{v_1} &= \frac{N_2}{N_1} = n & \frac{i_1}{i_2} &= \frac{v_2}{v_1} = n
 \end{aligned}$$


Ideal Transformers: Comments

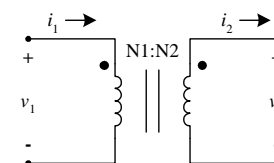

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n \qquad \frac{i_2}{i_1} = \frac{N_1}{N_2} = \frac{1}{n}$$

- Defining equations for ideal transformers do not include time
- The phasor domain equations are identical to the time domain
- The ideal transformer can not store energy
- Note direction of secondary current
- Sometimes only the turns ratio is given: $N_2/N_1 = n$

Ideal Transformers: The Dot Convention

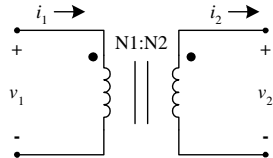


- The dot convention determines the polarity of the defining equations
- If v_1 and v_2 are both positive or both negative at the dotted terminals, use $+n$. Otherwise, use $-n$.
- If i_1 and i_2 both enter or both leave the dotted terminals, use $-n$. Otherwise, use $+n$.

Example 6: The Dot Convention for Ideal Transformers




Write the defining equations for each of the circuits shown above.

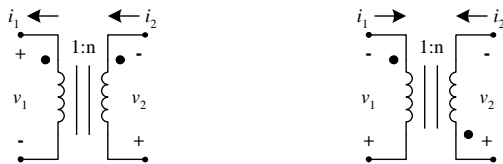Example 7: The Dot Convention for Ideal Transformers




Write the defining equations for each of the circuits shown above.

Ideal Transformer: Reflected Impedance

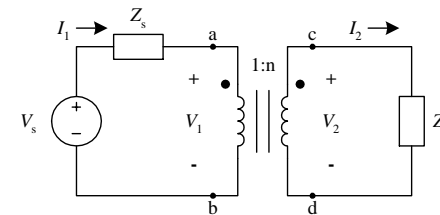

$$Z_R = \frac{V_1}{I_1} = \frac{V_2 \frac{1}{n}}{I_2 n} = \frac{V_2}{I_2} \frac{1}{n^2} = \frac{Z_L}{n^2}$$


Example 8: Ideal Transformers

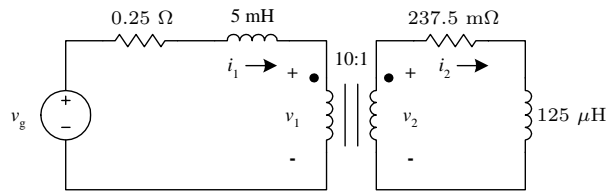

If $v_g = 2500 \cos(400t)$ V, find i_1 , v_1 , i_2 , and v_2 .

Example 8: Workspace

Example 9: Ideal Transformers

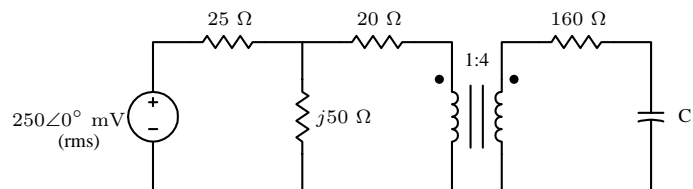

Find the value of C that maximizes the power absorbed by the 160Ω resistor. What is the average power delivered for this value of C ? Replace the resistor with a variable resistor and find the value that maximizes the power delivered? What is the maximum average power that can be delivered?

Example 9: Workspace (1)

Example 9: Workspace (2)
